



vifalio

FREE PRINTABLE GUIDE · US ELECTRICAL DRAWINGS

60+ SYMBOLS EXPLAINED

HOW TO READ ELECTRICAL DRAWINGS

Floor plans, wiring diagrams, schematics and one-line diagrams, made simple

- ✓ Outlet, switch and lighting symbols
- ✓ Home runs, switch legs and circuit numbers
- ✓ NEMA schematic symbols (contacts, coils, motors)
- ✓ One-line diagram and panel schedule
- ✓ Quiz with answers to practice




QUICK READING GUIDE

THE 4 KINDS OF ELECTRICAL DRAWINGS


Before reading symbols, know which drawing you are looking at.

FLOOR PLAN

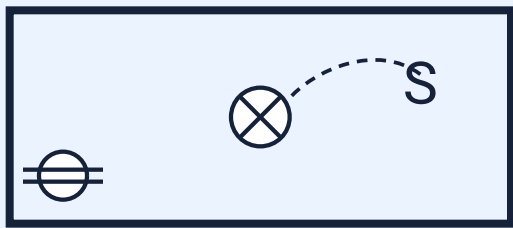


Shows WHERE each outlet, switch and light goes in the house. Used to install.

WIRING DIAGRAM

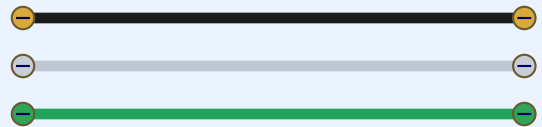

Shows HOW each wire connects, with real colors and terminals. Used to wire.

SCHEMATIC (LADDER)

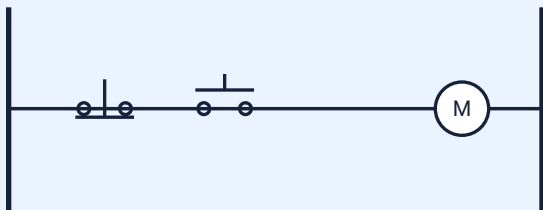

Shows how the circuit WORKS: contacts, coils and loads in rungs. Used to troubleshoot.

ONE-LINE



Shows the power path in one line: utility, meter, panels, big loads. Used to plan.



SAFETY FIRST

Breaker off, test before touching



NEC / ANSI

Common US symbols



PRO TIPS

From the field



vifalio.com

Free guide

QUICK READING GUIDE

OUTLET SYMBOLS

Receptacles on a US floor plan (ANSI style)



Duplex receptacle

Standard 120 V outlet, 2 plugs



GFCI receptacle

Ground-fault protected: baths, kitchens, outdoors



Weatherproof receptacle

Outdoor outlet with in-use cover



Switched receptacle

Half (or all) of the outlet controlled by a switch



Quad receptacle

Four plugs: two duplex in one box



240 V receptacle

Range, dryer or welder outlet



Floor receptacle

Outlet in a floor box



Tamper-resistant

TR outlet, required in homes (NEC 406.12)



SAFETY FIRST

Breaker off, test before touching



NEC / ANSI

Common US symbols



PRO TIPS

From the field



vifalio.com

Free guide

QUICK READING GUIDE

SWITCH SYMBOLS

The letter S is a switch: the small mark tells the type

S

Single-pole switch

Controls a light from one place

S₃

3-way switch

Two switches control the same light

S₄

4-way switch

Third (or more) control point between 3-ways

S_D

Dimmer switch

Adjusts the brightness

S_{OS}

Occupancy sensor

Turns on with movement

S_{WP}


Weatherproof switch

Outdoor or wet location



Switch leg

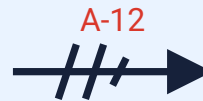Dashed line: which switch controls which light



Home run

Arrow to the panel; hash marks = number of wires; A-12 = panel A, circuit 12

**SAFETY FIRST**

Breaker off, test before touching

**NEC / ANSI**

Common US symbols

**PRO TIPS**

From the field



vifalio.com

Free guide

QUICK READING GUIDE

LIGHTING & DEVICE SYMBOLS

Fixtures, fans, detectors and boxes

**Ceiling fixture**

Light mounted on the ceiling

**Recessed light**

Can light / downlight

**Wall fixture**

Sconce or wall light

**Ceiling fan**

Fan with or without light kit

**Smoke detector**

Hard-wired, usually interconnected

**CO detector**

Carbon monoxide alarm

**Junction box**

Box where wires are spliced

**Thermostat**

Low-voltage HVAC control

**SAFETY FIRST**

Breaker off, test before touching

**NEC / ANSI**

Common US symbols

**PRO TIPS**

From the field


**vifalio.com**

Free guide

QUICK READING GUIDE

READING A REAL FLOOR PLAN

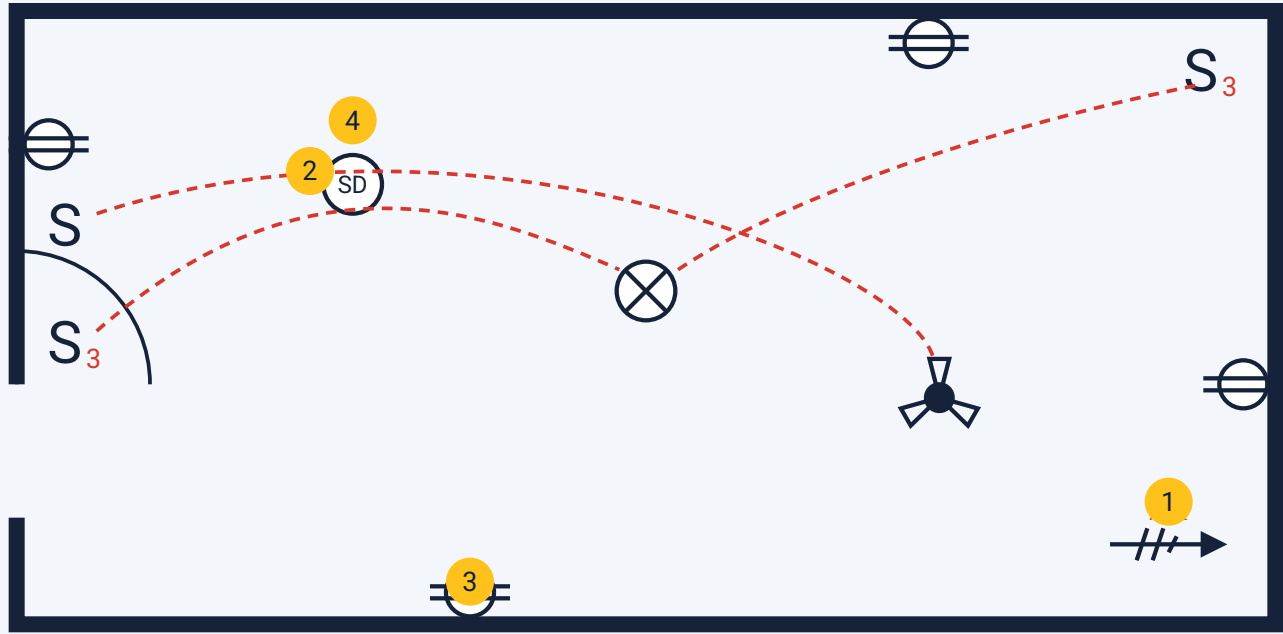A bedroom drawn the way you will see it on a blueprint.



- 1 Find the PANEL and the home run arrow: it tells the circuit (A-12).
- 2 Follow the dashed switch legs from each S to the lights it controls.
- 3 Count the receptacles on the walls and look for GFCI/WP notes.
- 4 Check the legend box of the drawing: drafters change symbols.


SAFETY FIRST

Breaker off, test before touching


NEC / ANSI

Common US symbols


PRO TIPS

From the field


vifalio.com

Free guide

QUICK READING GUIDE

HOME RUNS AND WIRE MARKS

The small marks on a line tell you how many wires are inside.

**Long mark**

Hot conductor (black or red)

Short mark

Neutral (white)

Mark with a dot

Ground (green or bare)

A-12

Panel A, circuit 12

2#12, #12G

Two 12 AWG wires plus one 12 AWG ground

3/4" C

3/4 inch conduit

**SAFETY FIRST**

Breaker off, test before touching

**NEC / ANSI**

Common US symbols

**PRO TIPS**

From the field

**vifalio.com**

Free guide

QUICK READING GUIDE

SCHEMATIC SYMBOLS (NEMA)

The ones you will find in motor controls and equipment diagrams.



Contact NO

Open until the coil is energized



Contact NC

Closed until the coil is energized



Pushbutton NO

Start



Pushbutton NC

Stop



Coil

Contactor or relay coil



Overload contact

Opens on overload



Timed contact

Closes after a delay



Pilot light

Indicator lamp

**SAFETY FIRST**

Breaker off, test before touching

**NEC / ANSI**

Common US symbols

**PRO TIPS**

From the field



vifalio.com

Free guide

QUICK READING GUIDE

SCHEMATIC SYMBOLS (NEMA)

The ones you will find in motor controls and equipment diagrams.



Fuse

Opens once on overcurrent



Circuit breaker

Trips on overcurrent, can be reset



Transformer

Changes the voltage



Motor

M inside a circle



Ground

Connection to earth



Resistor / heater

Heating element



Limit switch

Moved by the machine



Float switch

Moved by the liquid level

**SAFETY FIRST**

Breaker off, test before touching

**NEC / ANSI**

Common US symbols

**PRO TIPS**

From the field


**vifalio.com**

Free guide

QUICK READING GUIDE

ONE-LINE DIAGRAM OF A HOUSE

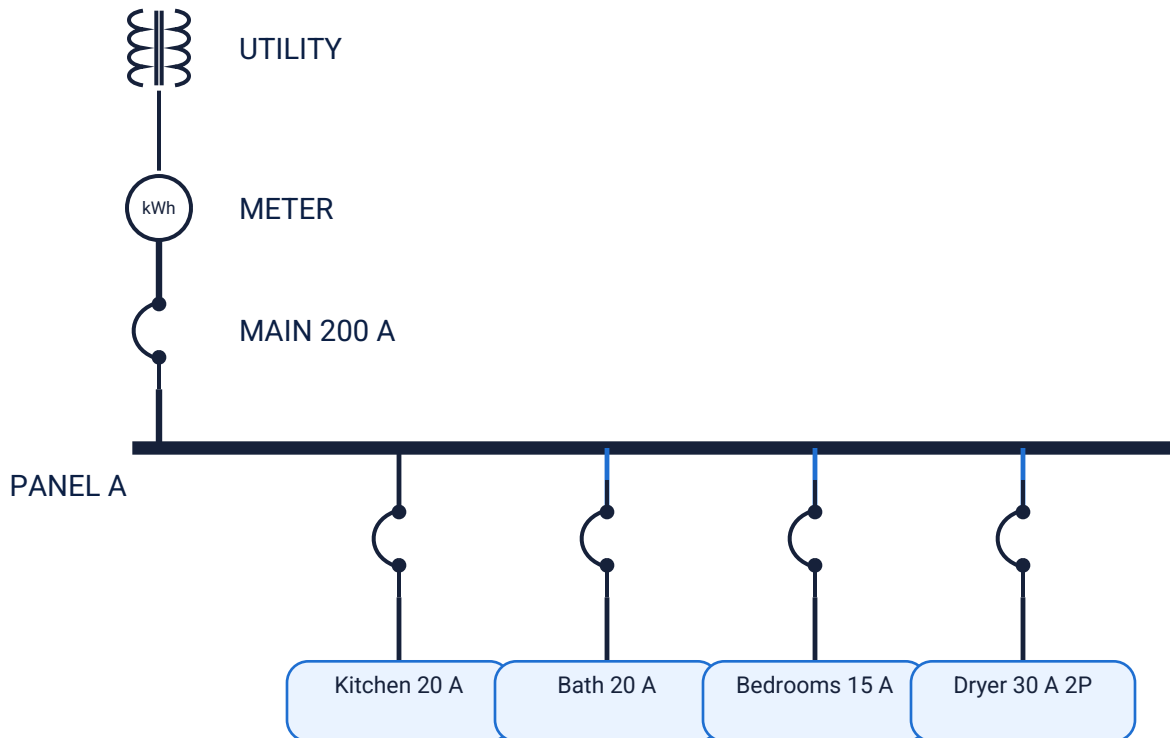How power gets from the street to each circuit.



- 1 Power comes from the utility transformer.
- 2 The meter measures the energy (kWh).
- 3 The main breaker protects the whole house.
- 4 Each branch breaker protects one circuit and its wire size.


SAFETY FIRST

Breaker off, test before touching


NEC / ANSI

Common US symbols


PRO TIPS

From the field



vifalio.com

Free guide

QUICK READING GUIDE

PANEL SCHEDULE

The table inside the panel door. It matches the numbers on the floor plan.

Ckt	Breaker	Wire	Description
1	20 A	12 AWG	Kitchen countertop GFCI
2	20 A	12 AWG	Kitchen countertop GFCI
3	20 A	12 AWG	Bathroom receptacles
4	15 A AFCI	14 AWG	Bedroom 1 lights & outlets
5	15 A AFCI	14 AWG	Bedroom 2 lights & outlets
6	20 A	12 AWG	Laundry receptacle
7-9	30 A 2P	10 AWG	Dryer 240 V
8-10	30 A 2P	10 AWG	Water heater 240 V
11	15 A	14 AWG	Smoke detectors
12	15 A AFCI	14 AWG	Living room

ABBREVIATIONS ON DRAWINGS

GFCI Ground-fault circuit interrupter

WP Weatherproof

EM Emergency

UNO Unless noted otherwise

C Conduit

NIC Not in contract

AFCI Arc-fault circuit interrupter

TR Tamper-resistant

NL Night light / unswitched

AFF Above finished floor (mounting height)

2P Two-pole (240 V) breaker

TYP Typical (same for all)



SAFETY FIRST

Breaker off, test before touching



NEC / ANSI

Common US symbols



PRO TIPS

From the field



vifalio.com

Free guide

QUICK READING GUIDE

PRACTICE: NAME THE SYMBOL

Write the name under each symbol. Answers at the bottom.

A



B



C



D



E



F



G



H



Answers:

A) GFCI receptacle B) 3-way switch C) Recessed light D) Smoke detector E) Switched receptacle F) 4-way switch G) Ceiling fan H) 240 V receptacle

**SAFETY FIRST**

Breaker off, test before touching

**NEC / ANSI**

Common US symbols

**PRO TIPS**

From the field

**vifalio.com**

Free guide

NOW YOU CAN READ THE PLAN

- ✓ Always start with the legend box of the drawing.
- ✓ Follow the home runs back to the panel.
- ✓ Match the circuit numbers with the panel schedule.
- ✓ Keep this guide on your phone for the job site.

Found this guide useful? Share it with a friend.

vifalio.com

**SAFETY FIRST**

Breaker off, test before touching

**NEC / ANSI**

Common US symbols

**PRO TIPS**

From the field

**vifalio.com**

Free guide